

Chapter V

Phase Locked Loops for High Frequency Transmitters and Receivers

By Mike Curtin

PLL Basics

A phase-locked loop is a feedback system combining a voltage controlled oscillator and a phase comparator so connected that the oscillator frequency (or phase) accurately tracks that of an applied frequency- or phase-modulated signal. Phase-locked loops can be used, for example, to generate stable output frequency signals from a fixed low-frequency signal. The phase locked loop can be analyzed in general as a negative feedback system with a forward gain term and a feedback term. A simple block diagram of a voltage-based negative-feedback system is shown in Figure 1.

 


Figure 1. Standard Negative-Feedback Control System Model

In a phase-locked loop, the error signal from the phase comparator is the difference between the input frequency or phase and that of the signal fed back. The system will force the frequency or phase error signal to zero in

the steady state. The usual equations for a negative-feedback system apply.

$$\text{Forward Gain} = G(s) \quad s = j\omega = j2\pi f$$

$$\text{Loop Gain} = G(s) \cdot H(s)$$

$$\text{Closed Loop Gain} = \frac{G(s)}{1 + G(s) \cdot H(s)}$$

Because of the integration in the loop, at low frequencies, the steady state gain, $G(s)$, is high

$$\text{and } \frac{V_O}{V_I}, \text{Closed Loop Gain} = \frac{1}{H}$$

The components of a PLL which contribute to the loop gain are as follows:

1. The Phase Detector (PD) and Charge Pump (CP).
2. The Loop Filter with a transfer function of $Z(s)$
3. The Voltage Controlled Oscillator (VCO) with a sensitivity of K_V/s
4. The Feedback Divider, $1/N$

 


Figure 2. Basic Phase Locked Loop Model

If a linear element like a four-quadrant multiplier is used as the phase detector, and the loop filter and VCO are also analog elements, this is called an analog, or linear PLL (LPLL). If a digital phase detector (EXOR gate or J-K flip flop) is used, and everything else stays the same, the system is called a digital PLL (DPLL).

If the PLL is built exclusively from digital blocks, without any passive components or linear elements, it becomes an all-digital PLL (ADPLL). Finally, with information in digital form, and the availability of sufficiently fast processing, it is also possible to develop PLLs in the software domain. The PLL function is performed by software and runs on a DSP. This is called a software PLL (SPLL).

Referring to Figure 2, a system for using a PLL to generate higher frequencies than the input, the VCO oscillates at an angular frequency of ω_D . A portion of this frequency/phase signal is fed back to the error detector, via a frequency divider with a ratio $1/N$. This divided-down frequency is fed to one input of the error detector. The other input in this example is a fixed reference frequency/phase. The error detector compares the signals at both inputs. When the two signal inputs are equal in phase and frequency, the error will be zero and the loop is said to be in a “locked” condition. If we simply look at the error signal, the following equations may be developed.

$$e(s) = F_{REF} - \frac{F_o}{N}$$

$$\begin{aligned} \text{When } e(s) = 0 &\Rightarrow \frac{F_o}{N} = F_{REF} \\ &\Rightarrow F_o = N \times F_{REF} \end{aligned}$$

In commercial PLLs, the phase detector and charge pump together form the error detector block. When $F \neq (N \times F_{REF})$, the error detector will output source/sink current pulses to the low pass

loop filter. This smoothes the current pulses into a voltage which in turn drives the VCO. The VCO frequency will then increase or decrease as necessary, by $(K_V \times \Delta V)$, where K_V is the VCO sensitivity in MHz/Volt and ΔV is the change in VCO input voltage. This will continue until $e(s)$ is zero and the loop is locked. The charge pump and VCO thus serves as an integrator, seeking to increase or decrease its output frequency to the value required so as to restore its input (from the phase detector) to zero.

 


Figure 3. VCO Transfer Function

The overall transfer function (CLG or Closed Loop Gain) of the PLL can be expressed simply by using the CLG expression for a negative feedback system as given above.

$$\frac{F_o}{F_{REF}} = \frac{\text{Forward Gain}}{1 + \text{Loop Gain}}$$

$$\text{Loop Gain, } GH = \frac{K_d \cdot K_v \cdot Z(s)}{N_s}$$

$$\text{Forward Gain, } G = \frac{K_d \cdot K_v \cdot Z(s)}{s}$$

When GH is much greater than 1, we can say that the closed loop transfer function for the PLL system is N and so $F_{OUT} = N \cdot F_{REF}$.

The loop filter is of a low-pass nature. It usually has one pole and one zero. The transient response of the loop depends on;

- 1) the magnitude of the pole/zero,
- 2) the charge pump magnitude,
- 3) the VCO sensitivity,
- 4) the feedback factor, N.

All of the above must be taken into account when designing the loop filter. In addition, the filter must be designed to be stable (usually a phase margin of $\pi/4$ is recommended). The 3-dB cutoff frequency of the response is usually called the loop bandwidth, B_w . Large loop bandwidths result in fast transient response. However, this is not always advantageous, as we shall see later, since there is a trade off between fast transient response and reference spur attenuation.

PLL Synthesizer Basic Building Blocks

It is possible to break up the PLL synthesizer into a number of basic building blocks. These have already been touched upon, but we will now deal with them in greater detail.

(i) The Phase Frequency

Detector, PFD

(ii) The Reference Counter, R

(iii) The Feedback Counter, N

The Phase Frequency Detector or PFD

The heart of a synthesizer is the phase detector or phase frequency detector. This is where the reference frequency signal is compared with the signal fed back from the VCO output and the resultant error is used to drive the loop filter and VCO. In a Digital PLL (DPLL) the phase detector or phase frequency detector is a logical element. The three most common implementations are :

(i) The EXOR gate

(ii) The J-K flip-flop

(iii) The phase frequency (PFD)

 


Figure 4. Typical PFD Using D-Type Flip Flops

Here we will consider only the PFD since this is the element used in the ADF41XX family of PLL synthesizers. The PFD differs from the EXOR gate and the J-K flip flop in that, its output is a function of both the frequency difference and phase difference between the two inputs.

Figure 4 shows one implementation of a PFD. It basically consists of two D-type flip flops, with one Q output enabling a positive current source and the other Q output enabling a negative current source. Let's assume in this design that the D-type flip flop is positive edge triggered. There are three possible states for the combination of UP and DOWN from the D-type flip flops. The state of 11, where both outputs are high, is disabled by the AND gate (U3) back to the CLR pins on the flip flops. The state of 00 (Q1, Q2) means that both P1 and N1 are turned off and the output, OUT is essentially in a high impedance state. The state 10 means that P1 is turned on, N1 is turned off and the output is at V+. The state of 01 means P1 is turned off, N1 is turned on and the output is at V-.

Lets consider how the circuit behaves if the system is out of lock and the frequency on +IN is much higher than the frequency on -IN. Figure 5 is a diagram which shows the relevant waveforms.

 


Figure 5. PFD Waveforms, Out of Frequency and Phase Lock

Since the frequency on +IN is much higher than on -IN, the output spends most of its time in the high state. The first rising edge on +IN sends the output high and this is maintained until the first rising edge occurs on -IN. In a practical system this means that the output to the VCO is driven higher resulting in an increase in frequency at -IN. This is exactly what we want.

If the frequency on +IN was much lower than on -IN, then we would get the opposite effect. The output at OUT would spend most of its time in the low condition. This would have the effect of driving the VCO in the negative direction and bringing the frequency at -IN much closer to that at +IN. In this way, locking is achieved.

Now let's look at the waveforms when the inputs are frequency locked and almost phase locked. Figure 6 is the diagram.

 


Figure 6. PFD Waveforms, Out of Phase Lock, In Frequency Lock

Since the phase on +IN is leading that on -IN, the output is a series of positive current pulses. These pulses will tend to drive the VCO so that the -IN signal become phase -aligned with the +IN signal.

When this occurs, if there was no delay element between U3 and the CLR inputs of U1 and U2, it would be possible for the OUT signal to be in high impedance mode, with neither positive or negative current pulses on the output. This would not be a good thing to happen. The VCO would drift until a significant phase error developed and started producing either positive or negative current pulses once again. Looked at over a relatively long period of time, the effect of this would be to have the output of the charge pump modulated by a signal that is a sub-harmonic of the PFD input reference frequency. Since this could be a low frequency signal it would not be attenuated by the loop filter and would result in very significant spurs in the VCO output spectrum. The phenomenon is known as the backlash effect and the delay element between the output of U3 and the CLR inputs of U1 and U2 ensures that it does not happen. With the delay element, even when the +IN and -IN are perfectly phase-aligned, there will still be a current pulse generated at the charge pump output. The duration of this delay is equal to the delay inserted at the output of U3 and is known as the anti-backlash pulse width.

The Reference Counter

In the classical Integer-N synthesizer, the resolution of the output frequency is determined by the reference frequency applied to the Phase Detector. So, for example, if 200kHz spacing is required (as in GSM phones), then the reference frequency must be 200kHz. However, getting a stable 200kHz frequency source is not easy and it makes more sense to take a good crystal-based high frequency source and divide it down. So, we could have a 10MHz Frequency Reference, divide this down by 50 and have the desired frequency spacing. This is shown in the diagram in Figure 7.

 


Figure 7. Using a Reference Counter in a PLL Synthesizer

The Feedback Counter, N

The N counter or N divider, as it is sometimes called, is the programmable element that sets the output frequency in the PLL. In fact, the N counter has become quite complex over the years. Instead of being a straightforward N counter it has evolved to include a prescaler which can have a dual modulus.

If we confine ourselves to the basic divide-by-N structure to feed back to the phase detector, we can run into problems if very high

frequency outputs are required. For example, let's assume that a 900MHz output is required with 10kHz spacing. We can use a 10MHz Reference Frequency, and set the R-Divider at 1000. Then, the N-value in the feedback would need to be around 90,000. This would mean at least a 17-bit counter. This counter would have to be capable of dealing with an input frequency of 900MHz. It makes sense to precede the programmable counter with a fixed counter element to bring the very high input frequency down to a range at which standard CMOS will operate. This is called the prescaler and is shown in Figure 8.

 


Figure 8. Basic Prescaler

However, using a standard prescaler introduces other complications. The system resolution is now degraded ($F_1 \times P$). The dual-modulus prescaler addresses this issue. The dual-modulus prescaler, shown below in Figure 9, gives the advantages of the standard prescaler without any loss in system resolution. A dual-modulus prescaler is a counter whose division ratio can be switched from one value to another by an external control signal. By using the dual-modulus prescaler with an A and B counter one can still maintain output resolution of F_1 . However, the following conditions must be met:

1. The output signal of both counters is HIGH if the counters have not timed out.
2. When the B counter times out, its output goes LOW and it immediately loads both counters to their preset values.
3. The value loaded to the B counter must always be greater than that loaded to the A counter.

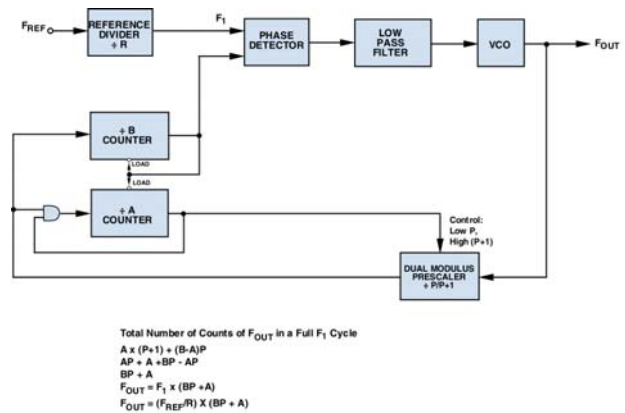


Figure 9. The Dual-Modulus Prescaler

Assume that the B counter has just timed out and both counters have been reloaded with the values A and B. Let's find the number of VCO cycles necessary to get to the same state again.

As long as the A counter has not timed out, the prescaler is dividing down by $P+1$. So, both the A and B counters will count down by 1 every time the prescaler counts $(P + 1)$ VCO cycles. This means the A counter will time out after $\{(P + 1) \times A\}$ VCO cycles. At this point the prescaler is switched to (divide-by-P). It is also possible to say that at this time

the B counter still has (B - A) cycles to go before it times out. How long will it take to do this: $\{(B - A) \times P\}$. The system is now back to the initial condition where we started. The total number of VCO cycles needed for this to happen is :

$$\begin{aligned} & \{(P + 1) \times A\} + \{(B - A) \times P\} \\ &= AP + A + BP - AP \\ &= \{(P \times B) + A\} \end{aligned}$$

When using a dual modulus prescaler, it is important to consider the lowest and highest value of N possible. What we really want here is the range over which it is possible to change N in discrete integer steps. Consider our expression for N: $N = BP + A$. To ensure a continuous integer spacing for N, A must be in the range 0 to (P - 1). Then, every time B is incremented there is enough resolution to fill in all the integer values. As we have already said for the dual modulus prescaler, B must be greater than or equal to A for the dual modulus prescaler to work. From these two conditions, we can say that the smallest division ratio possible while being able to increment in discrete integer steps is:

$$\begin{aligned} N_{MIN} &= (B_{min} \times P) + A_{min} \\ &= ((P-1) \times P) + 0 \\ &= P^2 - P \end{aligned}$$

The highest value of N is given by

$$N_{MAX} = (B_{max} \times P) + A_{max}$$

In this case A_{max} and B_{max} are simply

determined by the size of the A and B counters.

Now, let's take a practical example using the ADF4111.

Lets assume the prescaler is programmed to 32/33.

A counter: 6 bits means A can be $2^6 - 1 = 63$

B counter : 13 bits means B can be $2^{13} - 1 = 8191$

$$N_{MIN} = P^2 - P = 992$$

$$\begin{aligned} N_{MAX} &= (B_{max} \times P) + A_{max} \\ &= (8191 \times 32) + 63 \\ &= 262175 \end{aligned}$$

Fractional-N Synthesizers

Many of the emerging wireless communication systems have a need for faster switching and lower phase noise in the Local Oscillator. This is particularly true in GSM systems. We have seen that Integer-N synthesizers require a PFD frequency which is equal to the channel spacing. This can be quite low and thus necessitates a high N. This high N produces a phase noise that is proportionately high. The low PFD frequency in turn means a low loop bandwidth which limits the PLL lock time. If we could divide by a fraction in the feedback, then it would be possible to use a higher reference frequency and still achieve the desired channel spacing. This lower number would also mean lower phase noise. So, in theory, fractional-N

synthesis offer a means of improving both phase noise and lock time in PLL's. In fact it is possible to implement division by a fraction over a long period of time by alternately dividing by two integers (divide by 2.5 can be achieved by dividing successively by 2 and 3). So, how do we decide to divide by X or (X+1) (assuming that our fractional number is between these two values)? Well, we can take the fractional part of the number and allow it to accumulate at the Reference Frequency rate.

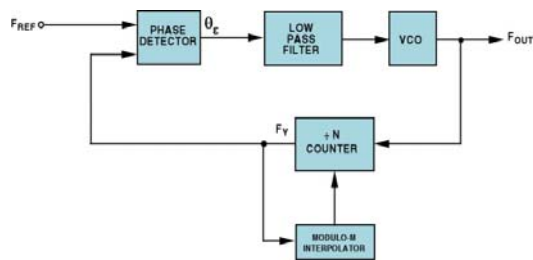


Figure 10. The Fractional-N Synthesizer

Since it is based on integer-N, the fractional-N PLL inherits many of the building blocks of its predecessor. The PFD, charge pump, loop filter, and VCO all work in the same way on both platforms. The N-divider is different, however. In a fractional-N PLL, the N-divider is broken up into the integer divider (N) and a modulus-M interpolator (M), which acts as the fraction function by toggling the N-divider. The interpolator is programmed with some value (f). The average division factor is now $N + f/M$ where:

$$0 < f < M$$

$$(N + f/M) = RF_{OUT} / F_{PFD}$$

This is the essence of fractional-N synthesis. It means that the PFD frequency can be larger than the RF channel resolution. In relation to the GSM-900 example, it may be instructive to examine how the fractional-N approach handles the generation of 900-MHz output signals with 200-kHz channel resolution. If a modulus M of 10 is available, F_{PFD} can be set to 2 MHz. N is programmed to 450, f is 0, and M is 10. To tune to 900.2 MHz RF_{OUT} , $N_{AVERAGE}$ must be 450.1, N is programmed to 450, f is 1, and M is 10. To achieve this, the N-divider is toggled under the control of the interpolator between N and N+1 and the average taken. What effectively occurs is that the N-divider divides by 450 nine times, and then divides by 451 once every 10 PFD cycles. The average over the 10 cycles of 450.1 is taken as $N_{AVERAGE}$, which is fed to the PFD. However, much complex circuitry is needed to implement this.

Interpolators can be implemented using the overflow bit of an accumulator. Alternatively, sigma-delta modulators are often employed for this task due to their averaging function and noise-shaping characteristics. In this case, every time an N value is presented to the PFD, it has been modulated by the sigma-delta modulator. This introduces spurs to the loop at F_{PFD}/M .

IMPORTANT SPECIFICATIONS IN PLL SYNTHESIZERS

Noise

In any oscillator design, frequency stability is of critical importance. In general, it is possible to separate stability into long-term stability and short-term stability. Long-term frequency stability is concerned with how the output signal varies over a long period of time (this can be hours, days or months). It is usually specified in Df/f for a given period of time and can be linear or exponential in nature.

Short-term stability, on the other hand, is concerned with variations that occur over a period of seconds or less. These variations can be random or periodic. We can use a spectrum analyzer to look at short-term stability of a signal. Figure 1 shows a typical spectrum.

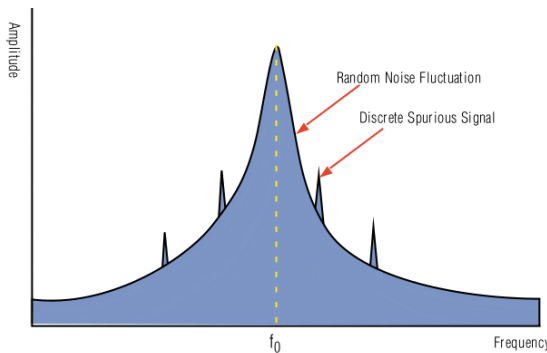


Figure 11. Short-term stability in oscillators

The discrete spurious components are non-random in nature and can be the result of known clock frequencies in the signal source, power line interference or mixer products.

The random noise fluctuation shown in Figure 11 is called phase noise. It can be due to thermal noise, shot noise or flicker noise in active and passive devices.

Phase Noise In Voltage Controlled Oscillators

Before we look at phase noise in a PLL system, it is worth considering the phase noise in a VCO. An ideal VCO would have no phase noise. If we looked at the output on a spectrum analyzer, we would see only one spectral line. In practice of course, this is not the case. There will be jitter on the output and, looked at on a spectrum analyzer, this will give rise to what we call phase noise. In terms of understanding phase noise it is useful to consider a phasor representation. Figure 2 shows the effect of superimposed noise voltages on a carrier signal. We call this effect phase noise.

 


Figure 12. Phasor Representation of Phase Noise

A signal of angular velocity, \mathbf{V}_0 , and peak amplitude V_{Spk} is shown. Superimposed on

this is an error signal of angular velocity, \mathbf{v}_m . Du_{rms} represents the rms value of the phase fluctuations and is expressed in rms degrees. In many radio systems there is an overall integrated phase error specification which must be met. This overall phase error is made up of the PLL phase error, the modulator phase error and the phase error due to base band components. In GSM, for example, the total allowed is 5 degrees rms. It is important that each of the contributing components are minimized. GSM designers like to keep the PLL phase error below 1 degree rms in the 200kHz frequency band around the carrier.

Leeson's Equation

Leeson developed an equation to describe the different noise components in a VCO.

$$L_{PM} \approx 10 \log \left[\frac{FkT}{A} \frac{1}{8Q_L^2} \left(\frac{f_o}{f_m} \right)^2 \right]$$

Where

L_{PM} is single-sideband phase noise density (dBc/Hz)

F is the device noise factor at operating power level A (linear)

k is Boltzmann's constant, 1.38×10^{-23} (J/K)

T is temperature (K)

A is oscillator output power (W)

Q_L is loaded Q (dimensionless)

f_o is the oscillator carrier frequency

f_m is the frequency offset from the carrier

For Leeson's equation to be valid, the following must be true:

f_m , the offset frequency from the carrier is greater than the 1/f flicker corner frequency; the noise factor at the operating power level is known;

the device operation is linear;

Q includes the effects of component losses, device loading and buffer loading;

A single resonator is used in the oscillator.

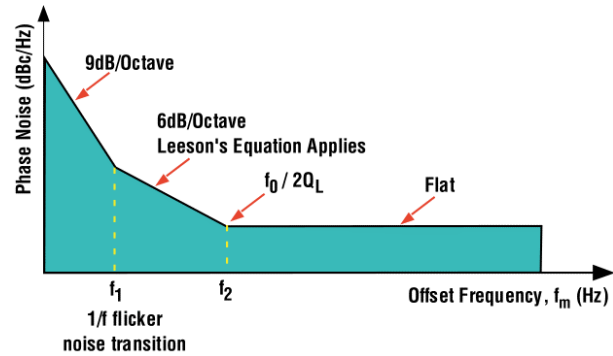


Figure 13. Phase Noise in a VCO vs.

Frequency Offset

Leeson's equation only applies between the 1/f flicker noise frequency (f_1) and a frequency past which amplified white noise dominates (f_2). This is shown in Figure 3. Typically, f_1 is less than 1kHz and should be as low as possible. The frequency f_2 is in the region of a few MHz. High-performance oscillators require devices specially selected for low 1/f transition frequency. Some guidelines to minimizing the phase noise in VCO's are:

1. Keep the tuning voltage of the varactor sufficiently high (typically between 3 and 3.8V)
2. Use filtering on the dc voltage supply.

3. Keep the inductor Q as high as possible. Typical off-the-shelf coils provide a Q of between 50 and 60.
4. Choose an active device that has minimal noise figure as well as low flicker frequency. The flicker noise can be reduced by the use of feedback elements
5. Most active device exhibit a bowl-shaped “Noise Figure vs Bias Current” curve. Use this information to choose the optimal operating bias current for the device.
6. Maximize the average power at the tank circuit output.
7. When buffering the VCO, use devices with the lowest possible Noise Figure.

$$\text{Closed Loop Gain} = \frac{G}{1 + GH}$$

$$G = \frac{K_d \cdot K_v \cdot Z(s)}{s}$$

$$H = \frac{1}{N}$$

$$\text{Closed Loop Gain} = \frac{\left(\frac{K_d \cdot K_v \cdot Z(s)}{s} \right)}{1 + \left(\frac{K_d \cdot K_v \cdot Z(s)}{N \cdot s} \right)}$$

Closing The Loop

We have looked at phase noise in a free-running VCO and considered how it can be minimized. Now, we will look at closing the loop and consider what effect this will have on phase noise.

 


Figure 14. PLL - Phase Noise contributors

Figure 14 shows the main phase noise contributors in a PLL as well as the system transfer function equations. The system may be described by the following equations.

The term, S_{REF} , is the noise that appears on the reference input to the phase detector. It is dependent on the reference divider circuitry and the spectral purity of the main reference signal. The term, S_N , is the noise due to the feedback divider appearing at the frequency input to the PD. The term, S_{CP} , is the noise due to the phase detector implementation. The last term, S_{VCO} , is the phase noise of the VCO as described by equations developed earlier.

The overall phase noise performance at the output is dependent on each of the terms described above. All the effects at the output are added in an rms fashion to give the total noise of the system. It is possible to write the following:

$$S_{TOT}^2 = X^2 + Y^2 + Z^2$$

S_{TOT}^2 is the total phase noise power at the output

X^2 is the noise power at the output due to S_N and S_{REF} .

Y^2 is the noise power at the output due to S_{CP}

Z^2 is the noise power at the output due to S_{VCO} . It can be clearly seen that the noise terms at the PD inputs, S_{REF} and S_N , will be operated on in the same fashion as F_{REF} and will be multiplied by the closed loop gain of the system.

$$X^2 = (S_{REF}^2 + S_N^2) \cdot \left(\frac{G}{1 + GH} \right)^2$$

At low frequencies, inside the loop bandwidth, $GH \gg 1$ and $X^2 = (S_{REF}^2 + S_N^2) \cdot N^2$

At high frequencies, outside the loop bandwidth,

$$G \ll 1 \text{ and } X^2 \Rightarrow 0$$

The contribution to the overall output noise due to the phase detector noise, S_{CP} , can be calculated by referencing S_{CP} back to the input of the PFD. The equivalent noise at the PD input is S_{CP}/K_d . This is then multiplied by the Closed Loop Gain. So:

$$Y^2 = S_{CP}^2 \cdot \left(\frac{1}{K_d} \right)^2 \cdot \left(\frac{G}{1 + GH} \right)^2$$

Finally, the contribution of the VCO noise, S_{VCO} , to the output phase noise is calculated in a similar manner. The forward gain this time is simply 1. Therefore the final output noise term can be described as:

$$Z^2 = S_{VCO}^2 \cdot \left(\frac{1}{1 + GH} \right)^2$$

G , the forward loop gain of the closed loop response, is usually a low pass function and it is very large at low frequencies and small at high frequencies. H is a constant, $1/N$. The bottom term of the above expression is therefore low pass. Therefore S_{VCO} is actually high pass filtered by the closed loop.

A similar description of the noise contributors in a PLL/VCO is described in Reference 1.

Recall that the closed loop response is a low pass filter with a 3 dB cutoff frequency, B_w , denoted the loop bandwidth. For frequency offsets at the output less than B_w , the dominant terms in the output phase noise response are X and Y , the noise terms due to reference noise, N counter noise and charge pump noise.

Keeping S_N and S_{REF} to a minimum, keeping K_d large and keeping N small will thus minimize the phase noise inside the loop bandwidth, B_w . Of course, keeping N small will not always be possible since this is what programs the output frequency.

For frequency offsets much greater than B_w , the dominant noise term is that due to the VCO, S_{VCO} . This is due to the high pass filtering of the VCO phase noise by the loop. A small value of B_w would be desirable as it would minimize the total integrated output noise (phase error). However a small B_w results in a slow transient response and increased contribution from the VCO phase noise inside the loop bandwidth. The loop bandwidth calculation therefore must trade off transient response versus total output integrated phase noise.

To show the effect of closing the loop in a PLL, it is possible to overlay the output of a free-running VCO with the output of a VCO as part of a PLL. This is shown in Figure 15 below. Note that the in-band noise of the PLL has been attenuated compared to the free-running VCO.

 


Figure 15. Phase Noise on a Free-Running VCO vs. VCO in a PLL

Phase Noise Measurement

One of the most common ways of measuring phase noise is with a high frequency spectrum analyzer. Figure 16 is a representation of what would be seen.

 


Figure 16. Phase Noise Definition

With the Spectrum Analyzer we can measure the one-sided spectral density of phase fluctuations per unit bandwidth. VCO phase noise is best described in the frequency domain where the spectral density is characterized by measuring the noise sidebands on either side of the output signal center frequency. Single sideband phase noise is specified in decibels relative to the carrier (dBc/Hz) at a given frequency offset from the carrier. The following equation describes this SSB phase noise.

$$S_C(f) = 10 \log \left(\frac{P_S}{P_{SSB}} \right), \text{ dBc} / \text{ Hz}$$

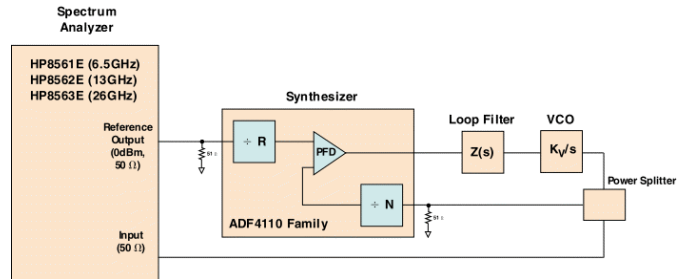


Figure 7. Measuring Phase Noise with a Spectrum Analyzer

The 10 MHz, 0dBm reference oscillator is available on the spectrum analyzer rear panel connector and it has excellent phase noise performance. The R divider, N divider and the phase detector are part of ADF4112 frequency synthesizer. These dividers are programmed serially under the control of a PC. The frequency and phase noise

performance are observed on the spectrum analyzer.

 


Figure 18. Typical Spectrum Analyzer Output

Figure 18 illustrates a typical phase noise plot of a PLL synthesizer using an ADF4112 PLL with a Murata VCO, MQE520-1880. The frequency and phase noise were measured in a 5 kHz span. The reference frequency used was $F_{REF} = 200$ kHz ($R=50$) and the output frequency was 1880 MHz ($N=9400$). If this was an ideal-world PLL synthesizer then a single discrete tone would be displayed along with the spectrum analyzer's noise floor. What is displayed here is the tone and the phase noise due to the loop components. The loop filter values were chosen to give a loop bandwidth of approximately 20 kHz. The flat part of the phase noise for frequency offsets less than the loop bandwidth is actually the phase noise as described by X^2 and Y^2 in the section "Closing The Loop" for cases where f is inside the loop bandwidth. It is specified at a 1 kHz offset. The value measured was -85.86 dBc/Hz. This is the phase noise power

in a 1 Hz bandwidth. This value is made up of the following:

- (i). *Relative power in dBc between the carrier and the sideband noise at 1kHz offset*
- (ii). *The spectrum analyzer displays the power for a certain resolution bandwidth (RBW). In the plot, a 10Hz RBW is used. To represent this power in a 1Hz bandwidth, $10\log(RBW)$ must be subtracted from the value in (i).*
- (iii). *A correction factor which takes into account the implementation of the RBW, the log display mode and detector characteristic must be added to the result in (ii).*

Phase noise measurement with the HP 8561E can be made quickly by using the marker noise function, MKR NOISE. This function takes into account the above three factors and displays the phase noise in dBc/Hz. The phase noise measurement above is the total output phase noise at the VCO output. If we want to estimate the contribution of the PLL device (noise due to phase detector, R&N dividers and the phase detector gain constant), we must divide our result by N^2 (or subtract $20 \cdot \log N$ from the above result). This gives a phase noise floor of $\{-85.86 - 20 \cdot \log(9400)\} = -165.3$ dBc/ Hz.

Normalized Phase Noise Floor

The PLL synthesizer Normalized Phase Noise Floor (or Figure of Merit, as it is sometimes known) in the phase noise normalized for a 1 Hz PFD frequency and is defined by the following equation:

$$PN_{SYNTH} = PN_{TOT} - 10 \log F_{PFD} - 20 \log N$$

PN_{SYNTH} is the Normalized Phase Noise Floor

PN_{TOT} is the measured phase noise at the PLL output

F_{PFD} is the PFD frequency

N is the value in the N counter

The Normalized Phase Noise Floor is a quick and convenient way of comparing the noise performance of PLL synthesizers.

Reference Spurs

In an integer- N PLL (where the output frequency is an integer multiple of the reference input), reference spurs are caused by the fact that there is continuous update of the charge pump output at the reference frequency rate. Let's once again consider the basic model for the PLL. This is shown again in Figure 19, below.

 


Figure 19. Basic PLL Model

When the PLL is in lock, the phase and frequency inputs to the PFD (f_{REF} and f_N) are essentially equal. In theory, one would expect that there would be no output from the PFD, in this case. However, this can create problems and so the PFD is designed so that, in the locked condition, the current pulses from the charge pump will typically look like Figure 20.

 


Figure 20. Output current pulses from the PFD Charge Pump

These pulses have a very narrow width but the fact that they exist means that the dc voltage driving the VCO is modulated by a signal of frequency f_{REF} . This produces what we call Reference Spurs in the RF output and these will occur at offset frequencies which are integer multiples of f_{REF} . It is possible to detect reference spurs using a spectrum analyzer. Simply increase the span to greater than twice the reference frequency. A typical plot is shown in Figure 11. In this case the reference frequency is 200kHz and the diagram clearly shows reference spurs at 6 200kHz from the RF output of 1880MHz. The level of these spurs is -90 dB. If we increased the span to greater than four times the

reference frequency then we would also see the spurs at $(2 \times f_{REF})$.

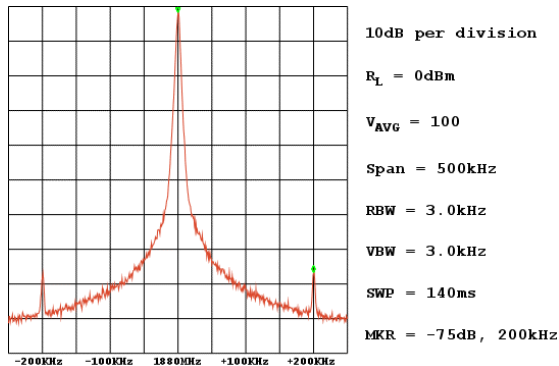


Figure 21. Output Spectrum showing Reference Spurs

Charge Pump Leakage Current

When the CP output from the synthesizer is programmed to the high impedance state, there should, in theory, be no leakage current flowing. In practice, of course, this is not the case and there are applications where the level of leakage current will have an impact on overall system performance. It is important to note that leakage current has a direct bearing on reference (PFD) spur level at the output of the PLL.

PLL Applications: Up-Conversion and Down-Conversion in Base Stations

The Phase Locked Loop allows stable high frequencies to be generated from a low-frequency reference. Any system that requires stable high frequency tuning can benefit from the PLL technique. The stable high frequency generated by the PLL is commonly known as a Local Oscillator (LO) and these are used in many systems like Wireless Basestations,

Wireless Handsets, Pagers, CATV Systems, Clock Recovery and Generation Systems. A good example of a PLL application is a GSM Handset or Basestation. Figure 22 shows the receive section of a GSM Basestation.

 


Figure 22. Signal Chain For GSM Base Station Receiver

In the GSM system, there are 124 channels (8 users per channel) of 200kHz width in the RF Band. The total bandwidth occupied is 24.8MHz, which must be scanned for activity. The handset has a TX range of 880MHz to 915MHz and an RX range of 925MHz to 960MHz. Conversely, the base station has a TX range of 925MHz to 960 MHz and an RX range of 880MHz to 915MHz. For our example lets just consider the base station transmit and receive sections. The frequency bands for GSM900 and DCS1800 Base Station Systems are shown in Table 1. Table 2 shows the channel numbers for the carrier frequencies (RF channels) within the frequency bands of Table 1. $F_l(n)$ is the center frequency of the RF channel in the lower band (R_x) and $F_u(n)$ is the corresponding frequency in the upper band (T_x).

	T_x	R_x
P-GSM900	935 –960MHz	890-915MHz
DCS1800	1805-1880MHz	1710-1785MHz
E-GSM900	925-960MHz	880-915MHz


Table 1. Frequency Bands for GSM900 and DCS1800 Base Station Systems

	R_x		T_x
PGSM900	$F_l(n) = 890 + 0.2 \times (n)$	$1 \leq n \leq 124$	$F_u(n) = F_l(n) + 45$
EGSM900	$F_l(n) = 890 + 0.2 \times (n)$	$0 \leq n \leq 124$	$F_u(n) = F_l(n) + 45$
	$F_l(n) = 890 + 0.2 \times (n-1024)$	$975 \leq n \leq 1023$	
DCS1800	$F_l(n) = 1710.2 + 0.2 \times (n - 512)$	$512 \leq n \leq 885$	$F_u(n) = F_l(n) + 95$

Table 2. Channel Numbering for GSM900 and DCS1800 Base Station Systems

The 900MHz RF input is filtered, amplified and applied to the first stage mixer. The other mixer input is driven from a tuned Local Oscillator (LO). This must scan the input frequency range to search for activity on any of the channels. The actual implementation of the LO is by means of the PLL technique already described. If the 1st Intermediate Frequency (IF) stage is centered at 240MHz, then the LO must have a range of 640MHz to 675MHz in order to cover the RF Input Band. When a 200kHz Reference Frequency is chosen, then it will be possible to sequence the VCO output through the full frequency range in steps of 200kHz. For example, when an output frequency of 650MHz is desired then N will have a value of 3250. This 650MHz LO will effectively check the 890MHz RF channel ($F_{RF} - F_{LO} = F_{IF}$ or $F_{RF} = F_{LO} + F_{IF}$) When N is incremented to 3251, the LO frequency will

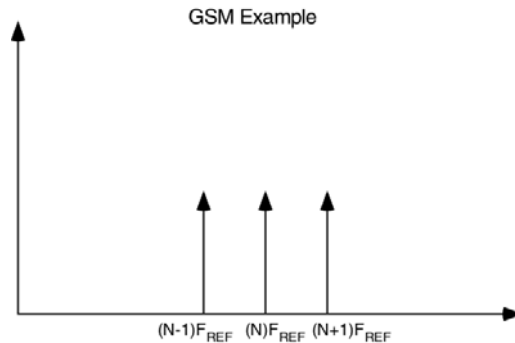now be 650.2MHz and the RF channel checked will be 890.2MHz. This is shown graphically in Figure 23.



$\Delta F = F_{REF}$
 For GSM: $F_{REF} = 200 \text{ kHz}$
 $F_{RF} = 880\text{MHz to } 915\text{MHz}$ for the Receiver
 If First IF is at 240MHz then LO must go from 640MHz to 675MHz.
 This Means N must vary from 3200 to 3375

Figure 23. Tuning Frequencies For GSM Base Station Receiver

channel spacing of 200kHz (the GSM standard), the reference input must be divided by 65, using the on-chip reference divider of the ADF4111.

The ADF4111 is an integer-N PLL frequency synthesizer, capable of operating up to an RF frequency of 1.2GHz. In this integer-N type of synthesizer, N can be programmed from 96 to 262,000 in discrete integer steps. In the case of the handset transmitter, where we need an output range of 880MHz to 915MHz., and where the internal reference frequency is 200kHz, the desired N values will range from 4400 to 4575.

The charge pump output of the ADF4111 (pin 2) drives the loop filter. This filter is a 1st Order lag lead type and it represented by Z(s) in the block diagram of Figure 2. In calculating the loop filter component values, a number of items need to be considered. In this example, the loop filter was designed so that the overall phase margin for the system would be 45 degrees. Other PLL system specifications are given below:

$$K_d = 5\text{mA}$$

$$K_v = 8.66\text{MHz/Volt}$$

$$\text{Loop Bandwidth} = 12\text{kHz.}$$

$$F_{\text{REF}} = 200\text{kHz}$$

$$N = 4500$$

Extra Reference Spur Attenuation of 10dB

All of these specifications are needed and used to come up with the loop filter components values shown in Figure 24.

The loop filter output drives the VCO which, in turn, is fed back to the RF input of the PLL

synthesizer and also drives the RF Output terminal. A T-circuit configuration with 18 ohm resistors is used to provide 50 ohm matching between the VCO output, the RF output and the RFIN terminal of the ADF4111.

In a PLL system, it is important to know when the system is in lock. In Figure 6, this is accomplished by using the MUXOUT signal from the ADF4111. The MUXOUT pin can be programmed to monitor various internal signal in the synthesizer. One of these is the LD or lock detect signal. When MUXOUT is chosen to select Lock Detect, it can be used in the system to trigger the output power amplifier, for example.

The ADF4111 uses a simple 4-wire serial interface to communicate with the system controller. The reference counter, the N counter and various other on-chip functions are programmed via this interface.

Receiver Sensitivity

Receiver sensitivity is the ability of the receiver to respond to a weak signal. Digital receivers use maximum bit error rate (BER) at a certain RF level to specify performance. In general, it is possible to say that device gains, noise figures, image noise and LO wideband noise all combine to produce an overall equivalent noise figure. This is then used to calculate the overall receiver sensitivity.

Wideband noise in the LO can elevate the IF noise level and thus degrade the overall noise factor. For example, wideband phase noise at

$F_{LO} + F_{IF}$ will produce noise products at F_{IF} . This directly impacts the receiver sensitivity. This wideband phase noise is primarily dependant on the VCO phase noise. Close in phase noise in the LO will also impact sensitivity. Obviously, any noise close to F_{LO} will produce noise products close to F_{IF} and impact sensitivity directly.

Receiver Selectivity

Receiver selectivity describes the tendency of a receiver to respond to channels adjacent to the desired reception channel. Adjacent Channel Interference (ACI) is a commonly used term in wireless systems which is also used to describe this phenomenon. When considering the LO section, the reference spurs are of particular importance with regard to selectivity. Figure 25 is an attempt to illustrate how a spurious signal at the LO, occurring at the channel spacing, can transform energy from an adjacent radio channel directly onto F_{IF} . This is of particular concern if the desired received signal is weak and the unwanted adjacent channel is strong, which can often be the case. So, the lower the reference spurs in the PLL, the better it will be for system selectivity.

 


Figure 25. Adjacent Channel Interference

Open Loop Modulation

Open Loop Modulation is a simple and inexpensive way of implementing FM. It also allows higher data rates than modulating in closed loop mode. For FM modulation, a closed loop method works fine but the data rate is limited by the loop bandwidth. A system which uses open loop modulation is the European cordless telephone system, DECT. The output carrier frequencies are in a range of 1.77GHz to 1.90GHz and the data rate is high; 1.152Mbps.

A block diagram of open loop modulation is shown in Figure 26. The principle of operation is as follows: The loop is closed to lock the RF output, $f_{OUT} = N \cdot f_{REF}$. The modulating signal is turned on and initially the modulation signal is simply the dc mean of the modulation. The loop is then opened, by putting the CP output of the synthesizer into high-impedance mode and the modulation data is fed to the Gaussian filter. The modulating voltage then appears at the VCO where it is multiplied by K_V . When the data burst finishes, the loop is returned to the closed loop mode of operation.

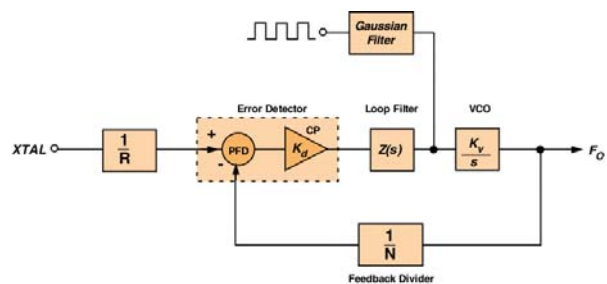


Figure 26. Block Diagram of Open Loop Modulation.

As the VCO usually has a high sensitivity (typical figures are between 20 and 80MHz/volt) any small voltage drift before the VCO will cause the output carrier frequency to drift. This voltage drift and hence the system frequency drift is directly dependant on the leakage current of the charge pump, CP, when in the high impedance state. This leakage will cause the loop capacitor to charge or discharge depending on the polarity of the leakage current. For example, a leakage current of 1nA would cause the voltage on the loop capacitor (1000pF for example) to charge by d_v/d_T . This, in turn, would cause the VCO to drift. So, if the loop is open for 1ms and the K_V of the VCO is 50MHz/Volt, then the frequency drift caused by 1nA leakage into a 1000pF loop capacitor would be 50kHz. In fact the DECT bursts are generally shorter (0.5ms) and so the drift will be even less in practice for the loop capacitance and leakage current used in our example. However, the example does serve to illustrate the importance of Charge Pump Leakage in this type of application

ADIsimPLL

Traditionally, PLL Synthesizer design relied on published application notes to assist in the design of the PLL loop filter. It was necessary to build prototype circuits to determine key performance parameters such as lock time, phase noise and reference spurious levels. Optimisation was limited to ‘tweaking’ component values on the bench and repeating

lengthy measurements. Using ADIsimPLL both streamlines and improves upon the traditional design process. ADIsimPLL is extremely user friendly and easy to use. Starting with the “new PLL wizard” a designer constructs a PLL by specifying the frequency requirements of the PLL, selecting an integer_N or Fractional-N implementation and then choosing from a library of PLL chips, library or custom VCO data, and a loop filter from a range of topologies. The wizard designs a loop filter and sets up the simulation program to display key parameters including phase noise, reference spurs, lock time, lock detect performance and others.

ADIsimPLL operates with spreadsheet-like simplicity and interactivity. The full range of design parameters such as loop bandwidth, phase margin, VCO sensitivity and component values can be altered with real-time update of the simulation results. This allows the user to easily tailor and optimise the design for their specific requirements. Varying the bandwidth, for example, enables the user to observe the trade-off between lock time and phase noise in real-time and with bench-measurement accuracy.

ADIsimPLL includes accurate models for phase noise, enabling reliable prediction of the synthesizer closed-loop phase noise. Users report excellent correlation between simulation and measurement.

ADIsimPLL also accurately simulates locking behaviour in the PLL, including the most significant non-linear effects. Unlike simple

linear simulators based on Laplace transform solutions, ADIsimPLL includes the effects of phase detector cycle slipping, charge pump saturation, curvature in the VCO tuning law and the sampling nature of the phase-frequency detector. As well as providing accurate simulation of frequency transients, giving detailed lock-time predictions for frequency and phase lock, ADIsimPLL also simulates the lock detect circuit. For the first time, designers can easily predict how the lock detect circuit will perform without having to resort to measurements.

The simulation engine in ADIsimPLL is fast, with all results typically updating ‘instantaneously’, even transient simulations. As well as providing an interactive environment that enables the design to be easily optimised, it also encourages the designer to explore the wide range of design options and parameters available.

Contrary to the traditional methods where to design, build and then measure parameters takes days, ADIsimPLL enables the user to change the PLL circuit design and observe instantly the performance changes.

ADIsimPLL allows the designer to work at a higher level and directly modify derived parameters such as the loop bandwidth, phase margin, pole locations, and the effects of the changes on performance are shown instantly (and without burning fingers with a soldering iron!).

If need be the designer can work directly at the component level and observe the effects of

varying individual component values.

ADIsimPLL Version 2 includes many enhancements including:

- the new PLL wizard now includes a short-form selector guide for choosing the PLL chip, displaying short-form data for all chips, with inbuilt links to the product pages on the Analog Devices website.

- Similar short-form selector guides are available for choosing the VCO device, and these contain links to detailed device data on vendor’s websites. The data in the selector guides can be sorted by any parameter.

- The chip-programming assistant enables rapid calculation of programming register values to set the chip any specified frequency. This is also great for checking channels that cannot be reached due to prescaler restrictions

- The range of loop filters has been expanded to include a 4-pole passive filter and a non-inverting active filter. As with all loop filter designs in ADIsimPLL, these models accurately include the thermal noise from resistors, the op-amp voltage and current noise, as well as predicting reference spurs resulting from the op-amp bias current.

- Phase jitter results can now be displayed in degrees, seconds or Error Vector Magnitude (EVM)

- It is now possible to simulate the power-up frequency transient.

- Support has been included for the new Analog Devices PLL chips with integrated VCO’s


With traditional design techniques, the evaluation of new devices requires construction, measurement and hand optimization of a prototype, which is a significant barrier to change and is often a key reason for the continual use of 'old' PLL chips. ADIsimPLL enables the rapid and reliable evaluation of new high performance PLL products from ADI. ADIsimPLL is the most comprehensive PLL Synthesizer design and simulation tool available today.

Simulations performed in ADIsimPLL include

all key non-linear effects that are significant in affecting PLL performance. ADIsimPLL removes at least one iteration from the design process, thereby speeding the design- to-market.

With ADIsimPLL you will get most PLL Synthesizer designs right first time - even the tough ones!

 Download your ADIsimPLL Software from <http://www.analog.com/pll>



The ADI Synthesizer Family

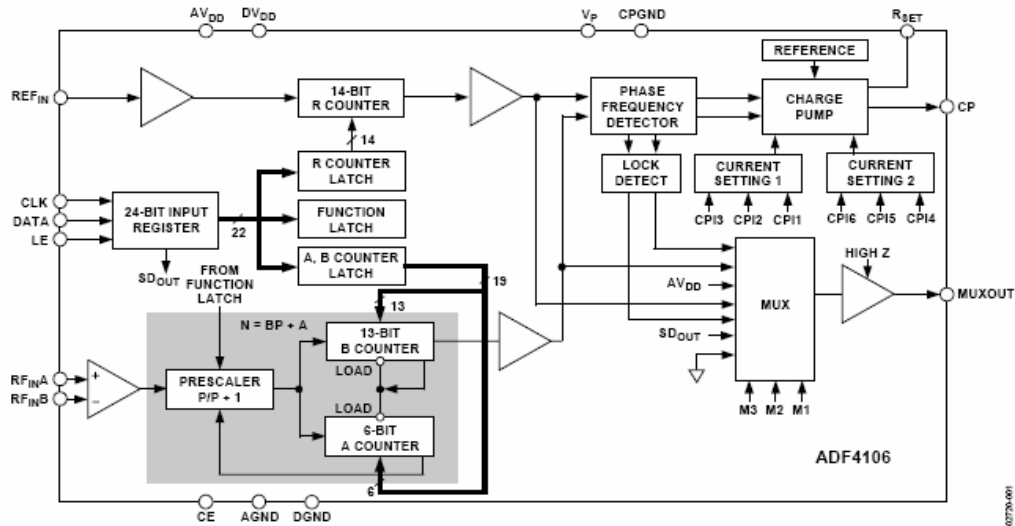


Figure 27. Block Diagram for the ADF4106

Below is a listing of the current ADI synthesizer family. It includes both single and dual integer-N and fractional-N devices. It also includes the new integrated VCO family (ADF4360 family).

ADF4110 Family

Single Proprietary Integer-N Synthesizers

ADF4001

This single synthesizer operates up to 200 MHz

ADF4110

This single synthesizer operates up to 550 MHz

ADF4111

This single synthesizer operates up to 1.2 GHz

ADF4112

This single synthesizer operates up to 3.0 GHz.

ADF4113

This single synthesizer operates up to 3.8 GHz.

ADF4106

This single synthesizer operates up to 6.0 GHz

ADF4107

This single synthesizer operates up to 7.0 GHz

ADF4007

This single synthesizer operates up to 7.5 GHz

ADF4116 Family

Single Second Source Integer-N Synthesizers

ADF4116

This single synthesizer operates up to 550 MHz. It is a second source to the LMX2306.

ADF4117

This single synthesizer operates up to 1.2 GHz. It is a second source to the LMX2316.

ADF4118	This single synthesizer operates up to 3.0 GHz. It is a second source to the LMX2326.
<u>ADF4212L</u>	Dual Proprietary Integer-N Synthesizer
ADF4212L	This dual synthesizer operates up to 510 MHz/2.4 GHz
<u>ADF4218L</u>	Dual Second Source Integer-N Synthesizer
ADF4218L	This dual synthesizer operates up to 510 MHz/ 3.0 GHz. It is a second source to the LMX2330L from National Semiconductor.
<u>ADF4153 Family</u>	Single Proprietary Fractional-N Synthesizer
ADF4153	This single synthesizer operates up to 4.0 GHz (16-pin package).
ADF4154	This single synthesizer operates up to 4.0 GHz (16-pin package).
ADF4156	This single synthesizer operates up to 6.4 GHz (16-pin package).
<u>ADF4252</u>	Dual Proprietary Fractional-N/Integer-N Synthesizer
ADF4252	This dual synthesizer operates up to 550MHz (Integer)/3.0 GHz (Fractional).
<u>ADF4360 Family</u>	Single Proprietary Integrated PLL Synthesizer and VCO
ADF4360-0	This single synthesizer operates from 2400 MHz to 2725 MHz
ADF4360-1	This single synthesizer operates from 2050 MHz to 2450 MHz
ADF4360-2	This single synthesizer operates from 1850 MHz to 2150 MHz
ADF4360-3	This single synthesizer operates from 1600 MHz to 1950 MHz
ADF4360-4	This single synthesizer operates from 1450 MHz to 1750 MHz
ADF4360-5	This single synthesizer operates from 1200 MHz to 1400 MHz
ADF4360-6	This single synthesizer operates from 1050 MHz to 1250 MHz
ADF4360-7	This single synthesizer operates from 350 MHz to 1800 MHz
ADF4360-8	This single synthesizer operates from 65 MHz to 400 MHz

References

1. *Mini-Circuits Corporation, "VCO Designers Handbook", 1996.*
2. *L.W. Couch, "Digital and Analog Communications Systems" Macmillan Publishing Company, New York, 1990.*
3. *P. Vizmuller, "RF Design Guide", Artech House, 1995.*

4. *R.L. Best, "Phase Locked Loops: Design, Simulation and Applications", 3rd Edition, McGraw Hill, 1997.*
5. *Brendan Daly, Comparing Integer-N And Fractional-N Synthesizers, Microwaves & RF, September 2001.*
6. *D.E. Fague, "Open Loop Modulation of VCOs for Cordless Telecommunications", RF Design, July 1994*